



# Advanced Digital Design

**PRESENTED BY:**

**Dr. Shasanka Sekhar Rout**

# Advanced Digital Design

**Pre-requisites:** Knowledge of Digital Fundamentals

## **Course Educational Objectives:**

- ✓ To make the students familiar with the basic concept of digital circuits
- ✓ Introduction to digital design with CMOS implementation
- ✓ Study of combinational & sequential logic circuits and advance digital design

## **Course Outcomes:**

- ❖ To understand and analyse the basic concept of digital logic circuits
- ❖ Able to design & demonstrate different combinational logic circuits & sequential logic circuits
- ❖ To understand CMOS implementation of digital design

# SYLLABUS

## Session 1

### Lecture: Basic Digital Circuits

- Basic Digital Circuits: Introduction, Principles, Working,
- Usage / Applications.

## Session 2

### Lecture: Combinational Circuits

- Logic Arrays
- NAND-NAND / NOR-NOR circuits
- Encoders and Decoders

## Session 3

### Lecture: Arithmetic Circuits

- 2's Complement
- Half and Full adders
- RCA,CLA,CSA

## Session 4 & 5

### Lecture: Logic Minimization

- Introduction to Various Logic Minimization techniques
- Quine McCluskey technique
- Shannon's reduction using relay switches

## Session 6

### Lecture: Logical Hazards

- Hazards and glitches
- Hazard elimination

## Session 7

### Lecture: Logic Families

- Introduction to different Logic families with their sub-families/types.
- TTL – NAND using TTL with working, different types of TTL families with features, usage.
- ECL – NAND using ECL with working, different types of ECL families with features, usage.
- CMOS – NAND using CMOS with working, Different types of CMOS families with features, usage.
- Comparison of speed and power of different families and sub-families/types.

## Session 8

### Lecture: Tristate and other circuits

- Tristate
- Muller-C
- AOI (And-Or-Inverter)
- Design of Logic Gates with CMOS technology: NOT, NAND, NOR, XOR.

## Session 9

### Lecture: Sequential Circuits

- ❖ Sequential Circuit Principles
- ❖ Types of Sequential Circuits
- ❖ Clock jitter, clock skew, timing parameters, propagation delays
- ❖ Latches
- ❖ Flip-flops

## Session 10 & 11

### Lecture: Counter Design and Frequency Division

- ❖ Counters: Introduction and types
- ❖ Designing of Counters using FSM approach: MOD-N, Binary, Decade
- ❖ Binary Counter as a Frequency divider
- ❖ Frequency division hazards

## Session 12

### Lecture: Registers

- ❖ Registers
- ❖ Shift Registers
- ❖ LIFO
- ❖ FIFO
- ❖ LFSR

## Session 13 & 14

### Lecture: Finite State Machines (FSM)

- ❖ Types of FSM
- ❖ Problem solving
- ❖ State reduction techniques

## Session 15 & 16

### Lecture: Static Timing Analysis

- ❖ Need of Static Timing Analysis of Digital Circuits
- ❖ Metastability
- ❖ Setup and Hold Violations
- ❖ Time Borrowing and Time Stealing

## Session 17 & 18

### Lecture: Asynchronous Circuits

- ❖ Introduction to multiple clock domain circuits
- ❖ Working across multiple clock domains
- ❖ Handshaking

## Session 19 & 20

### Lecture: Asynchronous to Synchronous Circuit Interaction

## Session 21 & 24

### Lecture: Case studies of Advanced Digital Design Circuits

- ❖ Several case studies like complex FSMs, Real life problems and their solutions, Pipelined Approaches for Communication Protocols or Recursive Operations, Design Optimization, Latency reduction, Development of Microporcessor / Microcontroller Design, Circuit Development for Data Encryption / Decryption Algorithms etc.

# REFERENCES

## **Text Book:**

1. Digital Design - Principles and Practices by John F Wakerly

## **Reference Books:**

1. An Engineering Approach to Digital Design by Fletcher

# Session 1

## Lecture: Basic Digital Circuits

- ✓ Basic Digital Circuits: Introduction, Principles, Working
- ✓ Usage / Applications

# Basic Digital Circuits

## Introduction:

- ✓ Digital circuits are the foundation of modern electronics, used in computers, communication devices, and embedded systems.
- ✓ Digital circuits operate using binary signals (0s and 1s) and are built using logic gates that perform basic operations.

### ➤ Basic Components of Digital Circuits are:

- ✓ Logic Gates (Building blocks of digital circuits)
- ✓ Combinational Circuits
- ✓ Sequential Circuits

| Inputs | AND | OR | NOT (A) | NAND | NOR | XOR | XNOR |
|--------|-----|----|---------|------|-----|-----|------|
| 0 0    | 0   | 0  | 1       | 1    | 1   | 0   | 1    |
| 0 1    | 0   | 1  | 0       | 1    | 0   | 1   | 0    |
| 1 0    | 0   | 1  | 1       | 1    | 0   | 1   | 0    |
| 1 1    | 1   | 1  | 0       | 0    | 0   | 0   | 1    |

### ➤ Digital circuits depends upon:

- ✓ Binary System and Logic Levels
- ✓ Number Systems Used in Digital Circuits
- ✓ Boolean Algebra and Simplification

# Basic Digital Circuits

## Digital Circuit Design Process:

1. Problem Definition – Identify the requirements
2. Truth Table Creation – Define inputs and outputs
3. Boolean Expression – Write the logic equation
4. Simplification – Minimize the logic equation
5. Circuit Implementation – Use logic gates to build the circuit
6. Testing & Simulation – Verify the design

## Technologies Used in Digital Circuits:

- **TTL (Transistor-Transistor Logic)** – Uses bipolar junction transistors (BJTs).
- **CMOS (Complementary Metal-Oxide-Semiconductor)** – Uses field-effect transistors (FETs) for low power consumption.
- **PLDs (Programmable Logic Devices)** – Include FPGA and CPLD for flexible digital design

# Basic Digital Circuits

## Principles & Working of Basic Digital Circuits:

- Digital circuits operate using binary signals (0s and 1s) and are based on fundamental principles that ensure reliable computation and processing.
- These principles form the backbone of digital electronics used in computers, communication devices, and embedded systems.

- ✓ 0 represents LOW (0V or ground)

- ✓ 1 represents HIGH (e.g., 5V, 3.3V, or 1.8V, depending on technology)

- ❖ Logic gates perform fundamental operations on binary inputs to produce a binary output.

- ❖ Basic Laws of Boolean Algebra:

- Identity Law:**  $A + 0 = A$ ,  $A \cdot 1 = A$

- Null Law:**  $A + 1 = 1$ ,  $A \cdot 0 = 0$

- Idempotent Law:**  $A + A = A$ ,  $A \cdot A = A$

- Complement Law:**  $A + A' = 1$ ,  $A \cdot A' = 0$

- De Morgan's Theorems:**

- $$(A \cdot B)' = A' + B'$$

- $$(A + B)' = A' \cdot B'$$



# Basic Digital Circuits

## Principle of Combinational and Sequential Logic:

### a) Combinational Circuits

- Output depends only on the present inputs.
- Examples: **Adders, Subtractors, Multiplexers, Decoders, Encoders.**

### b) Sequential Circuits

- Output depends on both present inputs and past states (memory).
- Uses Flip-Flops (FFs) to store information.
- Examples: **Counters, Registers, Finite State Machines (FSMs).**

## Synchronization and Timing:

- ❖ Digital circuits rely on **clock signals** to synchronize operations.
- ❖ Sequential circuits use **clock pulses** to transition between states.
- ❖ **Propagation delay** affects circuit speed and performance.
- The working of digital circuits is based on binary logic, logic gates, Boolean algebra, combinational/sequential logic, and clock signals.
- These circuits process, store, and transmit data efficiently, forming the backbone of modern computing and electronic devices.

# Basic Digital Circuits

## Usage / Applications:

Digital circuits are everywhere like control systems in cars, communication networks, and even medical equipment, which are the backbone of modern electronics.

### 1. Computing and Microprocessors:

- ◆ **Microprocessors & Microcontrollers**— The heart of all computers, smartphones.
- ◆ **Memory Units (RAM, ROM, Flash Storage)**— Used for data storage.
- ◆ **Arithmetic Logic Units (ALU)**— Mathematical and logical operations in CPUs.
- ◆ **Registers and Caches**— Store and process temporary data in processors.

**Example:** Laptop's CPU processes instructions using millions of digital logic gates.

### 2. Communication Systems

- ◆ **Digital Signal Processing (DSP)**— Used in audio, video, and wireless.
- ◆ **Modems and Network Devices**— Convert digital data into signals for transmission.
- ◆ **Error Detection & Correction Circuits**— Ensure data integrity in networks.
- ◆ **Encryption and Security Circuits**— Secure data transfer in communication systems.

**Example:** Wi-Fi router and 5G network use digital circuits for fast and secure data transmission.

# Basic Digital Circuits

## 3. Consumer Electronics:

- ◆ **Smartphones & Tablets**— Use microprocessors, memory, and display drivers.
- ◆ **Television & Displays**— Digital logic controls image processing.
- ◆ **Cameras & Image Processing**— Convert analog signals (light) into digital data.
- ◆ **Audio Processing (Speakers, Headphones, Music Systems)**— Uses DSP to enhance sound quality.

**Example:** Noise-canceling headphones use digital circuits to analyze and reduce unwanted sounds.

## 4. Industrial Automation and Robotics:

- ◆ **Programmable Logic Controllers (PLCs)**— Control industrial machinery.
- ◆ **Robotic Control Systems**— Process sensor data and control motors.
- ◆ **Digital Sensors & Actuators**— Used for precision in manufacturing.
- ◆ **Embedded Systems in IoT Devices**— Collect and process data for automation.

**Example:** Factory automation robots use digital circuits to follow programmed instructions.

# Basic Digital Circuits

## 5. Medical Electronics:

- ◆ **Digital Thermometers & Wearable Devices**– Convert temperature readings into digital values.
- ◆ **Heart Rate Monitors & ECG Machines**– Process signals from the body into digital form.
- ◆ **MRI & CT Scanners**– Use digital processing for imaging.
- ◆ **Hearing Aids & Pacemakers**– Use digital logic for real-time processing.

**Example:** A smartwatch tracks heart rate using digital circuits.

## 6. Automotive Electronics:

- ◆ **Engine Control Units (ECU)**– Manage fuel injection, emissions, and performance.
- ◆ **Automatic Transmission Systems**– Process sensor data to shift gears.
- ◆ **Anti-lock Braking System (ABS)**– Uses digital circuits for safety.
- ◆ **Infotainment Systems & Navigation (GPS)**– Convert digital data for display and control.

**Example:** Your car's dashboard screen and parking sensors rely on digital circuits.

# Basic Digital Circuits

## 7. Aerospace and Defense:

- ◆ **Radar & Satellite Communication**– Uses digital signal processing for tracking and communication.
- ◆ **Autopilot Systems in Aircraft**– Process sensor data for navigation.
- ◆ **Military Encryption Systems**– Secure communication using digital circuits.
- ◆ **Missile Guidance & Defense Systems**– Digital processors analyze and track targets.

**Example:** A fighter jet's radar system relies on digital circuits for precise tracking.

## 8. Smart Home & Internet of Things (IoT):

- ◆ **Home Automation (Smart Lights, AC, Locks)**– Controlled by digital circuits.
- ◆ **Digital Assistants (Alexa, Google Home, Siri)**– Process voice commands using digital circuits.
- ◆ **Surveillance & Security Systems**– Digital cameras and sensors detect motion.
- ◆ **Wearable IoT Devices**– Track health and fitness data.

**Example:** A smart thermostat adjusts your home temperature using digital circuits.

# Session 2

## Lecture: Combinational Circuits

- ✓ Logic Arrays
- ✓ NAND-NAND / NOR-NOR circuits
- ✓ Encoders and Decoders

# Combinational Circuits

- Logic circuits for digital systems may be **combinational** or **sequential**.
- A **combinational circuit** consists of logic gates whose outputs at any time are determined from only the present combination of inputs.
- In contrast, **sequential circuits** employ storage elements in addition to logic gates that means the outputs depends on present inputs and past outputs.



- For  $n$  input variables, there are  $2^n$  possible combinations of the binary inputs.
- Example of combinational circuit: Adders, Subtractors, Logic arrays, MUX, DEMUX, Encoders, Decoders etc.

# Combinational Circuits

## Logic Arrays:

- A Logic Array is a structured arrangement of logic gates designed to perform multiple logical or arithmetic operations simultaneously.
- They are commonly used in digital systems for arithmetic processing, data routing, and logic functions.
- They follow a predefined architecture that allows for scalability and efficient design.

## Types of Logic Arrays:

1. Programmable Logic Array (PLA)
2. Programmable Array Logic (PAL)
3. Field Programmable Gate Array (FPGA)
4. Gate Arrays (ASICs and Standard Cell Designs)



# Combinational Circuits

## 1. Programmable Logic Array (PLA):

- A **PLA** is a configurable combinational circuit where both the AND and OR gates are programmable. It allows for **custom logic function implementation** in a single chip.



### Structure:

- Input variables go into an **AND gate array**, which generates product terms.
- The outputs of the AND gate array feed into an **OR gate array** to produce the sum of products for the required Boolean functions.
- The output of the OR gate goes to an XOR gate, where the other input can be programmed to receive a signal equal to either logic 1 or logic 0.
- The output is inverted when the XOR input is connected to 1 (since  $x \oplus 1 = x'$ ).
- The output does not change when the XOR input is connected to 0 (since  $x \oplus 0 = x$ ).

# Combinational Circuits

## Advantages:

- Highly flexible (both AND and OR planes are programmable).
- Can implement multiple logic functions in a compact form.

**Example:** Used in custom digital logic design for memory addressing and arithmetic circuits.

**Problem:** Implement the following two Boolean functions with a PLA:

$$F_1 = AB' + AC + A'BC'$$


$$F_2 = (AC + BC)'$$

## Solution:

*PLA Programming Table*

| Product Term |   | Inputs |   |   | Outputs        |                |
|--------------|---|--------|---|---|----------------|----------------|
|              |   |        |   |   | (T)            | (C)            |
|              |   | A      | B | C | F <sub>1</sub> | F <sub>2</sub> |
| AB'          | 1 | 1      | 0 | — | 1              | —              |
| AC           | 2 | 1      | — | 1 | 1              | 1              |
| BC           | 3 | —      | 1 | 1 | —              | 1              |
| A'BC'        | 4 | 0      | 1 | 0 | 1              | —              |

# Combinational Circuits

 

PLA with three inputs, four product terms, and two outputs

# Combinational Circuits

## 2. Programmable Array Logic (PAL):

- A **PAL** is similar to a PLA but with a fixed OR gate array and a programmable AND gate array. It is easier to manufacture and use than a PLA.



### Advantages:

- Faster than PLA due to fixed OR gates.
- Simpler and cost-effective.

**Example:** Used in control systems and microcontroller interfacing.

- ✓ Because only the AND gates are programmable, the PAL is easier to program than, but is not as flexible as, the PLA.

# Combinational Circuits

**Problem:** Implement the following Boolean functions with a PAL:

$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$


$$\begin{aligned} z &= ABC' + A'B'CD' + AC'D' + A'B'C'D \\ &= w + AC'D' + A'B'C'D \end{aligned}$$

**Solution:**

*PAL Programming Table*

| Product Term | AND Inputs |   |   |   | w | Outputs                   |
|--------------|------------|---|---|---|---|---------------------------|
|              | A          | B | C | D |   |                           |
| 1            | 1          | 1 | 0 | — | — | $w = ABC' + A'B'CD'$      |
| 2            | 0          | 0 | 1 | 0 | — |                           |
| 3            | —          | — | — | — | — |                           |
| 4            | 1          | — | — | — | — | $x = A + BCD$             |
| 5            | —          | 1 | 1 | 1 | — |                           |
| 6            | —          | — | — | — | — |                           |
| 7            | 0          | 1 | — | — | — | $y = A'B + CD + B'D'$     |
| 8            | —          | — | 1 | 1 | — |                           |
| 9            | —          | 0 | — | 0 | — |                           |
| 10           | —          | — | — | — | 1 | $z = w + AC'D' + A'B'C'D$ |
| 11           | 1          | — | 0 | 0 | — |                           |
| 12           | 0          | 0 | 0 | 1 | — |                           |

# Combinational Circuits

 

# Combinational Circuits


## 3. Field Programmable Gate Array (FPGA):

- An **FPGA** is an advanced form of logic array where both combinational and sequential circuits can be implemented using programmable logic blocks.

### Advantages:

- Highly reconfigurable and reusable.
- Used in prototyping and hardware acceleration.

 **Example:** Used in AI, image processing, networking, and real-time processing applications.



# Combinational Circuits


## 4. Gate Arrays (ASICs and Standard Cell Designs):

- Gate arrays are pre-designed logic cells that are connected based on specific design requirements. These are used in **Application-Specific Integrated Circuits (ASICs)** for high-performance and mass production.

### Advantages:

- Optimized for performance and power efficiency.
- Ideal for high-volume production (e.g., mobile processors, GPUs).

 **Example:** Used in smartphones, gaming consoles, and automotive electronics.







# Combinational Circuits
 
## NAND-NAND / NOR-NOR circuits:

- ❖ NAND and NOR gates are **Universal gates**, meaning they can be used to design any logic gates and implement any Boolean function or logic circuit.
- ❖ By structuring digital circuits using only **NAND** or **NOR** gates, we achieve cost-effective, efficient, and reliable designs in digital systems.
- ✓ A **NAND-NAND circuit** is a combinational logic circuit where logic functions are implemented using only **NAND gates**.
- ✓ A **NOR-NOR circuit** follows the same principle but only uses **NOR gates** to implement logic functions



| INPUT |   | OUTPUT |
|-------|---|--------|
| A     | B | Q      |
| 0     | 0 | 1      |
| 0     | 1 | 1      |
| 1     | 0 | 1      |
| 1     | 1 | 0      |

 


| INPUT |   | OUTPUT |
|-------|---|--------|
| A     | B | Q      |
| 0     | 0 | 1      |
| 0     | 1 | 0      |
| 1     | 0 | 0      |
| 1     | 1 | 0      |


# Combinational Circuits

**NAND-NAND circuits:**


**NOT:**

 

**AND:**

 


**OR:**

 


# Combinational Circuits

**NAND-NAND circuits:**


**NOR:**

 

**EXOR:**

 


**EXNOR:**

 


# Combinational Circuits

**NOR-NOR circuits:**


**NOT:**

 

**OR:**

 


**AND:**

 


# Combinational Circuits

**NOR-NOR circuits:**


**NAND:**

 

**EXOR:**

 

**EXNOR:**

 


# Combinational Circuits
 
## NAND & NOR Implementation:


**Ex:**  $F = AB + CD$

$$\begin{aligned} F &= AB + CD \\ &= \overline{\overline{AB + CD}} \\ &= \overline{\overline{AB} \cdot \overline{CD}} \end{aligned}$$



**Ex:**  $F = (A + B)(C + D)$
 
$$\begin{aligned} F &= (A + B) \cdot (C + D) \\ &= \overline{\overline{(A + B) \cdot (C + D)}} \\ &= \overline{\overline{(A + B)} + \overline{(C + D)}} \end{aligned}$$




# Combinational Circuits

## Encoders and Decoders:

Encoders and decoders are essential combinational circuits used for **data conversion, signal transmission, and control applications** in digital electronics.
 
### Encoders:

- An encoder is a digital circuit that performs the inverse operation of a decoder.
- An encoder has  $2^n$  (or fewer) input lines and  $n$  output lines.



# Combinational Circuits

## Encoders (8-to-3):

*Truth Table of an Octal-to-Binary Encoder*

| Inputs |       |       |       |       |       |       |       | Outputs |     |     |
|--------|-------|-------|-------|-------|-------|-------|-------|---------|-----|-----|
| $D_0$  | $D_1$ | $D_2$ | $D_3$ | $D_4$ | $D_5$ | $D_6$ | $D_7$ | $x$     | $y$ | $z$ |
| 1      | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0       | 0   | 0   |
| 0      | 1     | 0     | 0     | 0     | 0     | 0     | 0     | 0       | 0   | 1   |
| 0      | 0     | 1     | 0     | 0     | 0     | 0     | 0     | 0       | 1   | 0   |
| 0      | 0     | 0     | 1     | 0     | 0     | 0     | 0     | 0       | 1   | 1   |
| 0      | 0     | 0     | 0     | 1     | 0     | 0     | 0     | 1       | 0   | 0   |
| 0      | 0     | 0     | 0     | 0     | 1     | 0     | 0     | 1       | 0   | 1   |
| 0      | 0     | 0     | 0     | 0     | 0     | 1     | 0     | 1       | 1   | 0   |
| 0      | 0     | 0     | 0     | 0     | 0     | 0     | 1     | 1       | 1   | 1   |

These conditions can be expressed by the following Boolean output functions:

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$


The encoder can be implemented with three OR gates.



# Combinational Circuits
 
## Decoders:

- ❖ A decoder is a combinational circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines.




- ❖ The decoders presented here are called  $n$ -to- $m$ -line decoders, where  $m \leq 2^n$ .
 
## 2-to-4-Line Decoder:

In 2-to-4-line decoder circuit, the two inputs are decoded into four outputs, each representing one of the minterms of the two input variables.

The two inputs are represented by  $A$  and  $B$  and outputs are represented by  $D_0$ ,  $D_1$ ,  $D_2$  and  $D_3$ .




Block diagram

# Combinational Circuits

## 2-to-4-Line Decoder:

| Inputs   |          | Outputs               |                       |                       |                       |
|----------|----------|-----------------------|-----------------------|-----------------------|-----------------------|
| <i>A</i> | <i>B</i> | <i>D</i> <sub>0</sub> | <i>D</i> <sub>1</sub> | <i>D</i> <sub>2</sub> | <i>D</i> <sub>3</sub> |
| 0        | 0        | 1                     | 0                     | 0                     | 0                     |
| 0        | 1        | 0                     | 1                     | 0                     | 0                     |
| 1        | 0        | 0                     | 0                     | 1                     | 0                     |
| 1        | 1        | 0                     | 0                     | 0                     | 1                     |


Truth table

 

Logic diagram

# Combinational Circuits


## 2-to-4-Line Active Low Decoder:

 

Block diagram

| Inputs |   | Outputs        |                |                |                |
|--------|---|----------------|----------------|----------------|----------------|
| A      | B | D <sub>0</sub> | D <sub>1</sub> | D <sub>2</sub> | D <sub>3</sub> |
| 0      | 0 | 0              | 1              | 1              | 1              |
| 0      | 1 | 1              | 0              | 1              | 1              |
| 1      | 0 | 1              | 1              | 0              | 1              |
| 1      | 1 | 1              | 1              | 1              | 0              |

Truth table

 


Logic diagram

# Combinational Circuits
 
## 3-to-8-Line Decoder:

In 3-to-8-line decoder circuit, the three inputs are decoded into eight outputs, each representing one of the minterms of the three input variables.




*Truth Table of a Three-to-Eight-Line Decoder*

| Inputs   |          |          | Outputs               |                       |                       |                       |                       |                       |                       |                       |
|----------|----------|----------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|
| <i>x</i> | <i>y</i> | <i>z</i> | <i>D</i> <sub>0</sub> | <i>D</i> <sub>1</sub> | <i>D</i> <sub>2</sub> | <i>D</i> <sub>3</sub> | <i>D</i> <sub>4</sub> | <i>D</i> <sub>5</sub> | <i>D</i> <sub>6</sub> | <i>D</i> <sub>7</sub> |
| 0        | 0        | 0        | 1                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     |
| 0        | 0        | 1        | 0                     | 1                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     |
| 0        | 1        | 0        | 0                     | 0                     | 1                     | 0                     | 0                     | 0                     | 0                     | 0                     |
| 0        | 1        | 1        | 0                     | 0                     | 0                     | 1                     | 0                     | 0                     | 0                     | 0                     |
| 1        | 0        | 0        | 0                     | 0                     | 0                     | 0                     | 1                     | 0                     | 0                     | 0                     |
| 1        | 0        | 1        | 0                     | 0                     | 0                     | 0                     | 0                     | 1                     | 0                     | 0                     |
| 1        | 1        | 0        | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 1                     | 0                     |
| 1        | 1        | 1        | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 1                     |

# Combinational Circuits



## 3-to-8-Line Decoder:

 

Three-to-eight-line decoder

  
## Multiplexers:

- A **multiplexer** is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line.
- The selection of a particular input line is controlled by a set of selection lines.
- Normally, there are  $2^n$  input lines and  $n$  selection lines whose bit combinations determine which input is selected.
- A multiplexer is also called a **data selector**, since it selects one of many inputs and steers the binary information to the output line.


 
## Two-to-One-line Multiplexer:

- A two-to-one-line multiplexer connects one of two 1-bit sources to a common destination, as shown in Fig.
- The circuit has two data input lines, one output line, and one selection line  $S$ .




Block diagram

| $S$ | $Y$   |
|-----|-------|
| 0   | $I_0$ |
| 1   | $I_1$ |

Function table


$$Y = I_0\bar{S} + I_1S$$

 

Logic diagram

 
## Four-to-One-line Multiplexer:

- Each of the four inputs,  $I_0$  through  $I_3$ , is applied to one input of an AND gate.
- Selection lines  $S_1$  and  $S_0$  are decoded to select a particular AND gate.
- The outputs of the AND gates are applied to a single OR gate that provides the one-line output.



| $S_1$ | $S_0$ | $Y$   |
|-------|-------|-------|
| 0     | 0     | $I_0$ |
| 0     | 1     | $I_1$ |
| 1     | 0     | $I_2$ |
| 1     | 1     | $I_3$ |


Function table

 


$$Y = I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0$$



 **Example:** Construct a  $16 \times 1$  multiplexer with two  $8 \times 1$  and one  $2 \times 1$  multiplexers.




 **Example:** Construct a  $16 \times 1$  multiplexer with five  $4 \times 1$  multiplexers.





**Example:** Implement the following Boolean function with a multiplexer.

$$F(x, y, z) = \sum(1, 2, 6, 7)$$

 

  
## De-multiplexers:

- A de-multiplexer performs the reverse operation of multiplexer; it takes single input and distributes it over several outputs.
- A decoder with enable input can function as a de-multiplexer - a circuit that receives information from a single line and directs it to one of  $2^n$  possible output lines.
- The selection of a specific output is controlled by the bit combination of  $n$  selection lines.
- A de-multiplexer is also called a **data distributor**, since it transmits the same data to different destinations.


 
## 1-to-4 Line De-multiplexer:

- A 1-to-4 line de-multiplexer has a single input ( $D$ ), two selection lines ( $S_1$  and  $S_0$ ) and four outputs ( $Y_0$  to  $Y_3$ ).
- The input data goes to any one of the four outputs at a given time for a particular combination of select lines.




| Data Input | Select Inputs |       | Outputs |       |       |       |
|------------|---------------|-------|---------|-------|-------|-------|
| D          | $S_1$         | $S_0$ | $Y_3$   | $Y_2$ | $Y_1$ | $Y_0$ |
| D          | 0             | 0     | 0       | 0     | 0     | D     |
| D          | 0             | 1     | 0       | 0     | D     | 0     |
| D          | 1             | 0     | 0       | D     | 0     | 0     |
| D          | 1             | 1     | D       | 0     | 0     | 0     |

$$Y_0 = \bar{S}_1 \bar{S}_0 D$$

$$Y_1 = \bar{S}_1 S_0 D$$


$$Y_2 = S_1 \bar{S}_0 D$$

$$Y_3 = S_1 S_0 D$$

 
 
## 1-to-8 Line De-multiplexer:

- A 1-to-8 de-multiplexer consists of single input **D**, three select inputs **S<sub>2</sub>**, **S<sub>1</sub>** and **S<sub>0</sub>** and eight outputs from **Y<sub>0</sub>** to **Y<sub>7</sub>**.
- It distributes one input line to one of 8 output lines depending on the combination of select inputs.



$$Y_0 = \bar{S}_2 \bar{S}_1 \bar{S}_0 D$$

$$Y_1 = \bar{S}_2 \bar{S}_1 S_0 D$$

$$Y_2 = \bar{S}_2 S_1 \bar{S}_0 D$$

$$Y_3 = \bar{S}_2 S_1 S_0 D$$

$$Y_4 = S_2 \bar{S}_1 \bar{S}_0 D$$


$$Y_5 = S_2 \bar{S}_1 S_0 D$$

$$Y_6 = S_2 S_1 \bar{S}_0 D$$

$$Y_7 = S_2 S_1 S_0 D$$

| Data Input | Select Inputs  |                |                | Outputs        |                |                |                |                |                |                |                |
|------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| D          | S <sub>2</sub> | S <sub>1</sub> | S <sub>0</sub> | Y <sub>7</sub> | Y <sub>6</sub> | Y <sub>5</sub> | Y <sub>4</sub> | Y <sub>3</sub> | Y <sub>2</sub> | Y <sub>1</sub> | Y <sub>0</sub> |
| D          | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | D              |
| D          | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 0              | 0              | D              | 0              |
| D          | 0              | 1              | 0              | 0              | 0              | 0              | 0              | 0              | D              | 0              | 0              |
| D          | 0              | 1              | 1              | 0              | 0              | 0              | 0              | D              | 0              | 0              | 0              |
| D          | 1              | 0              | 0              | 0              | 0              | 0              | D              | 0              | 0              | 0              | 0              |
| D          | 1              | 0              | 1              | 0              | 0              | D              | 0              | 0              | 0              | 0              | 0              |
| D          | 1              | 1              | 0              | 0              | D              | 0              | 0              | 0              | 0              | 0              | 0              |
| D          | 1              | 1              | 1              | D              | 0              | 0              | 0              | 0              | 0              | 0              | 0              |

## 1-to-8 Line De-multiplexer:

 

# THANK YOU

